

Question 1: [5 Marks]

Consider an inverter with the following characteristics,

$$V_{LS} = 0.8V, V_{TW} = 0.1V, V_M = -1.6V, V_{NMH} = 0.35V, \text{ and } V_{NML} = 0.35V$$

Draw the voltage transfer curve for this inverter assuming the curve is piecewise linear. Please show all critical voltages on the drawing.

$$V_{LS} = 0.8V \quad V_{TW} = 0.1V \quad V_M = -1.6V \quad V_{NMH} = 0.35V \quad V_{NML} = 0.35V$$

$$V_{LS} = V_{OH} - V_{OL} = 0.8V \quad \text{--- (1)}$$

$$V_{TW} = V_{IH} - V_{IL} = 0.1V \quad \text{--- (2)}$$

For ideal inverter VTC

$$V_M = \frac{V_{OH} - V_{OL}}{2} = -1.6V \quad \text{--- (3)}$$

$$V_M = \frac{V_{IH} - V_{IL}}{2} = -1.6V \quad \text{--- (4)}$$


by solving (1) with (3) & (2) with (4)

$$V_{OH} = -1.2V$$

$$V_{OL} = -2V$$

$$V_{IH} = -1.55V$$

$$V_{IL} = -1.65V$$

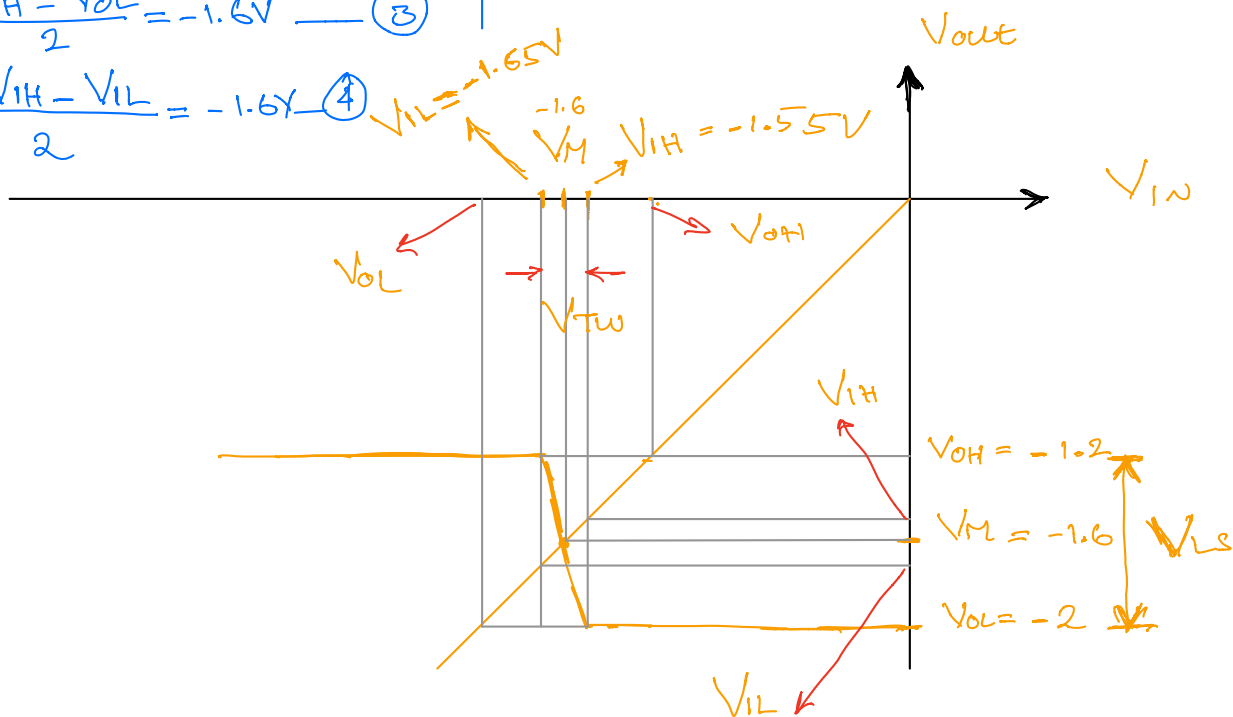

Question 2: [5 Marks]

- Draw cross section of a typical Schottky diode constructed on p-substrate and isolated with reverse biased junction.
- Design a level shifted 2-input AND gate using only diodes and resistors. The gate must conform to the following specifications,

$$V_{OH} = 0.87V, V_{OL} = -4V, P(OL) = 9.733mW, V_{CC} = 4V, \text{ and } V_{EE} = -4V$$

$$V_{OH} = 0.87V \quad V_{OL} = -4V \quad P(OL) = 19.46mW$$

$$V_{CC} = 4V \quad V_{EE} = -4V \rightarrow \text{It should be } -V_{EE} = -4V$$

To design means to find values of R_L & R_H

$$V_{OH} = I R_L - V_{EE}$$

$$I = \frac{V_{CC} - V_{D(ON)} + V_{EE}}{R_H + R_L}$$

$$V_{OH} = \left(\frac{V_{CC} - V_{D(ON)} + V_{EE}}{R_H + R_L} \right) R_L - V_{EE}$$

$$\frac{R_L}{R_H + R_L} = \frac{V_{OH} + V_{EE}}{V_{CC} - V_{D(ON)} + V_{EE}} = \frac{0.87 + 4}{4 - 0.7 + 4} = 0.667$$

$$\frac{R_L}{R_H + R_L} = 0.667 \quad \text{--- (1)}$$

$$V_{OH} = V_{CC} - I R_H - V_{D(ON)}$$

$$= V_{CC} - \left(\frac{V_{CC} - V_{D(ON)} + V_{EE}}{R_H + R_L} \right) R_H - V_{D(ON)}$$

$$\frac{R_H}{R_H + R_L} = \frac{V_{CC} - V_{D(ON)} - V_{OH}}{V_{CC} - V_{D(ON)} + V_{EE}} = \frac{4 - 0.7 - 0.87}{4 - 0.7 + 4} = 0.333$$


$$\frac{R_H}{R_H + R_L} = 0.333 \quad \text{--- (2)}$$

By dividing (1) by (2)

$$\frac{R_L}{R_H} = \frac{0.667}{0.333} = 2 \Rightarrow$$


$$\boxed{R_L = 2 R_H}$$

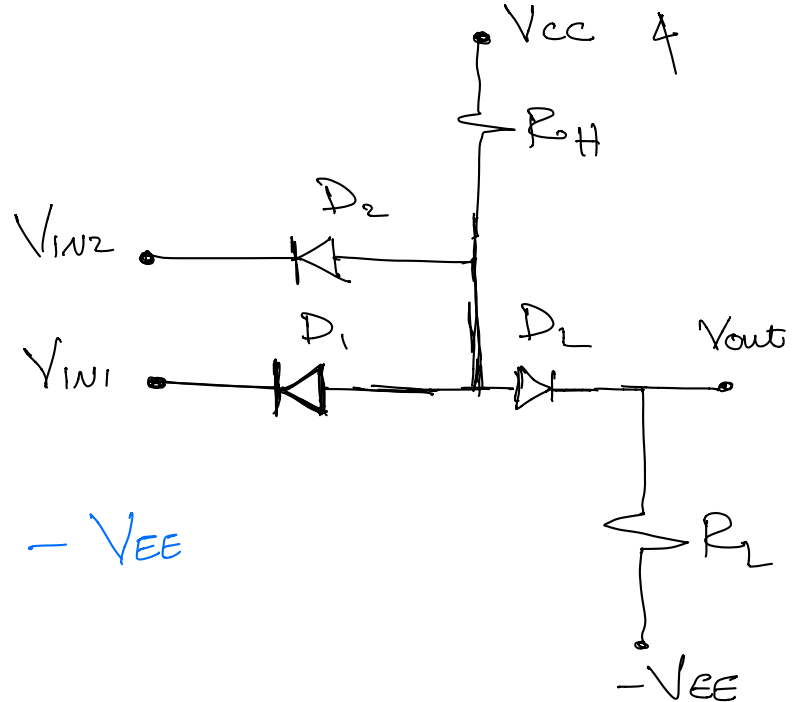we can choose any values for R_L & R_H that as long as $R_L = 2 R_H$



Consider the following RTL NOT gate. Assume $V_{BE}(SAT) = 0.8V$, $V_{CE}(SAT) = 0.2V$, and $\beta_F = 20$. Find the following.

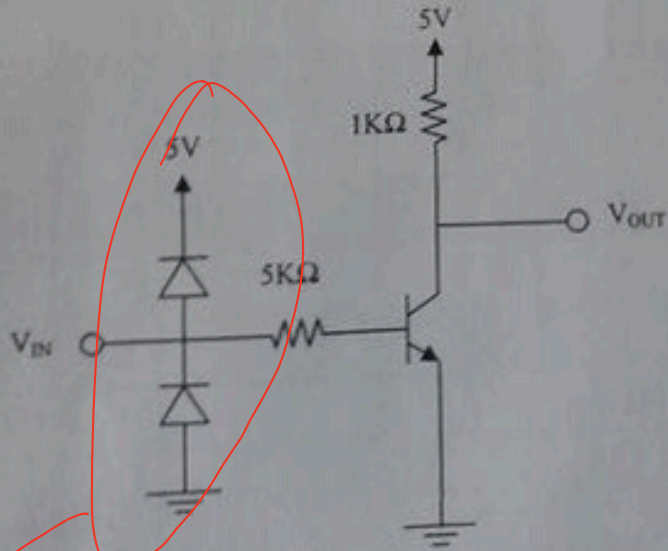
- Maximum fan-out
- Average power dissipation with maximum fan-out



This part means V_{IN} range is $0 \leq V_{IN} \leq 5$

a

For V_{IN} is high V_{OUT} is low

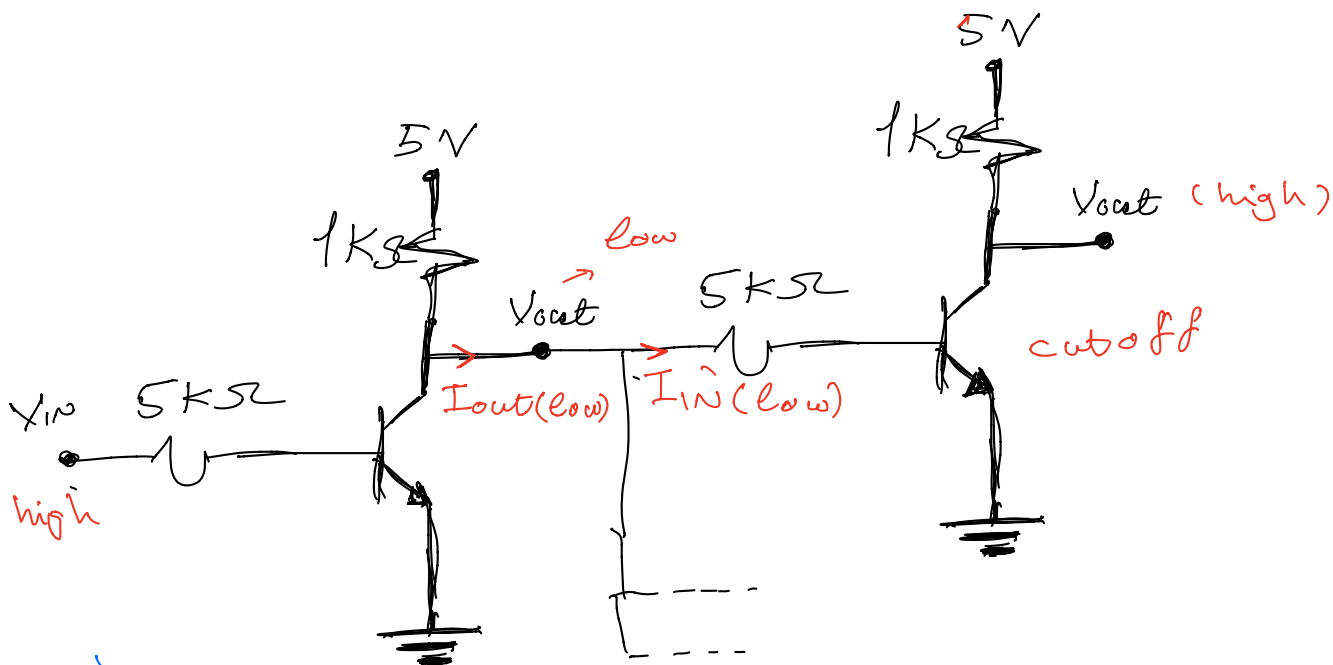


$$I_{IN}^{(low)} = 0$$

$$\Rightarrow N_{low} = \frac{I_{out}^{(low)}}{I_{IN}^{(low)}} = \infty$$

Therefore The maximum fanout depends on N_{high}

For V_{in} is low V_{out} is high

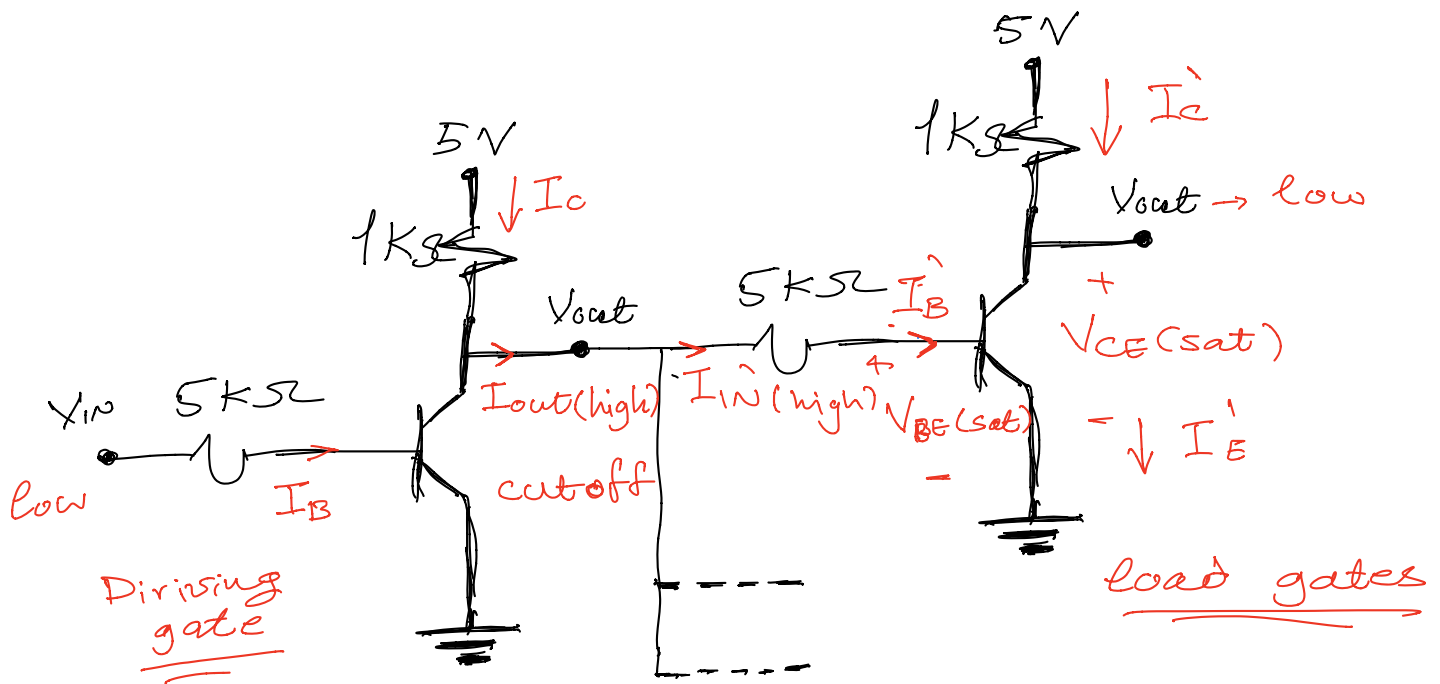

$$N_{max} = N_{high}(max)$$

*The maximum fan-out can be found when the input for the load gates is the minimum input that can be considered as high input which is V_{IH}

$$N_{max} = \frac{I_{out}(high)}{I_{in}(high)}$$


$$I_{out}(high) = I_c = \frac{5 - V_{IH}}{1k}$$

$$I_{in}(high) = I_B = \frac{V_{IH} - V_{BE}(sat)}{5k}$$

$$\begin{aligned} V_{IH} &= 5k \times I_B + V_{BE}(sat) \\ &= 5k \times \frac{I_c}{\beta_f} + V_{BE}(sat) \end{aligned}$$

$$= \frac{5k}{\beta_f} \left(\frac{5 - V_{CE}(sat)}{1k} \right) + V_{BE}(sat)$$
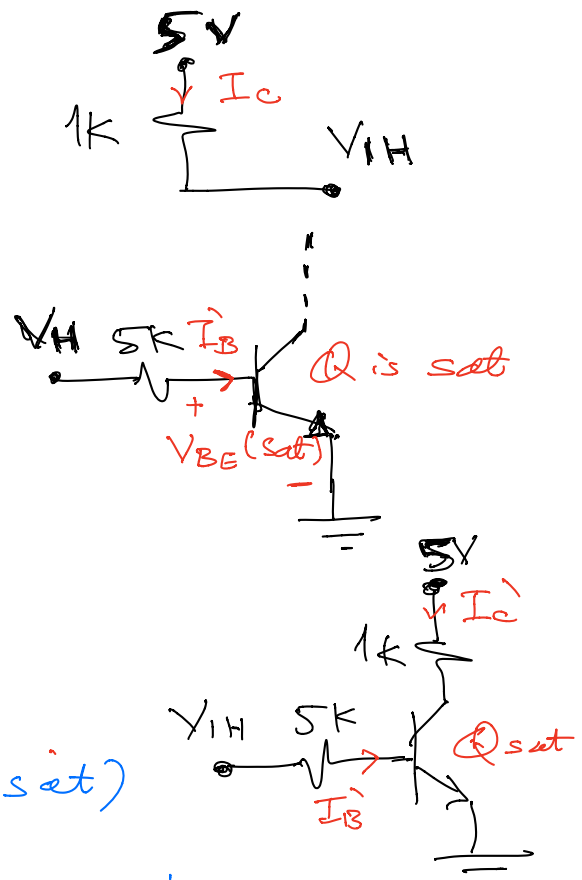
$$V_{IH} = \frac{5k}{20} \left(\frac{5 - 0.2}{1k} \right) + 0.8 = 2V$$



$$I_{out}(high) = \frac{5 - 2}{1k} = 3mA$$

$$I_{in}(high) = \frac{2 - 0.8}{5k} = 0.24mA$$

$$N_{max} = \frac{3mA}{0.24mA} = 12.5$$

∴ The maximum fan-out is 12

[b]

$$P_{cc(avg)} = \frac{P_{cc(OH)} + P_{cc(OL)}}{2}$$


$$= \left(\frac{I_{cc(OH)} + I_{cc(OL)}}{2} \right) V_{cc}$$

$$I_{cc(OL)} = I_C = \frac{5 - V_{CE(sat)}}{1k} = \frac{5 - 0.2}{1k} = 4.8mA$$

$$I_{cc(OH)} = \frac{5 - V_{BE(sat)}}{1k + \frac{5k}{N}}$$

The maximum fan-out $N=12$
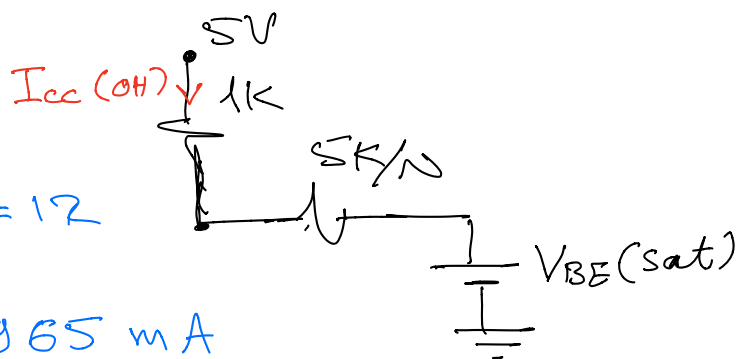
$$I_{cc(OH)} = \frac{5 - 0.8}{1k + \frac{5k}{12}} = 2.965mA$$



$$P_{cc(avg)} = \left(\frac{2.965mA + 4.8mA}{2} \right) (5) = 19.4mW$$